

3 Hours

Total Marks: 80


Note:

- Question No. 1 is compulsory.
- Answer any **three** from the remaining five questions.
- Assume suitable data if necessary and justify the same.

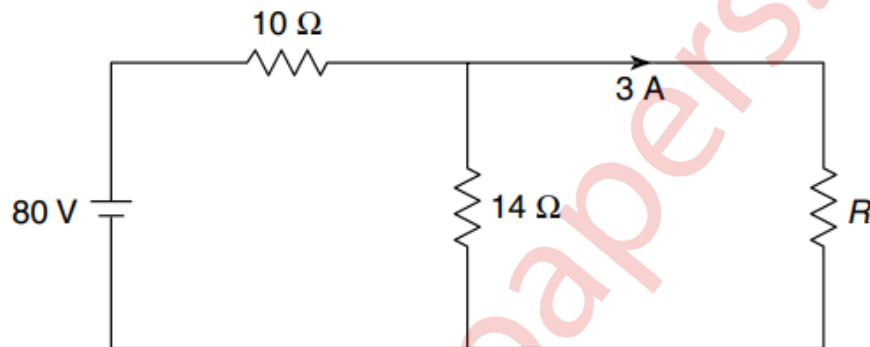Q1 Each question carries five marks


20M

a Determine the resistance 'R' in the following circuit




b What are the restrictions on pole and zero locations for Transfer Functions?

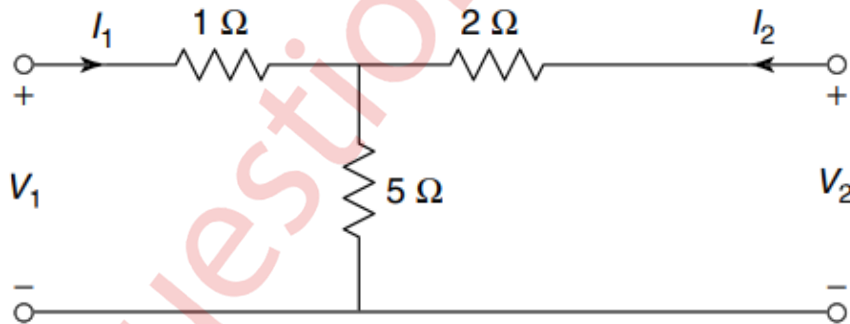
c For the given network, determine the transmission parameters



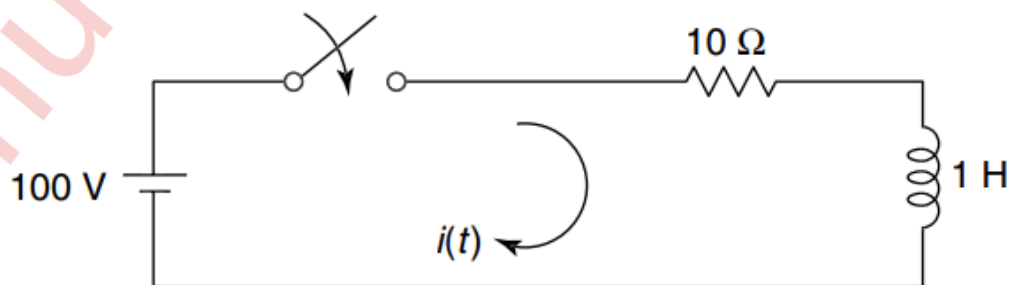
d In the given network switch is closed at $t=0$. With zero current in the inductor, find i and $\frac{di}{dt}$ at $t=0+$



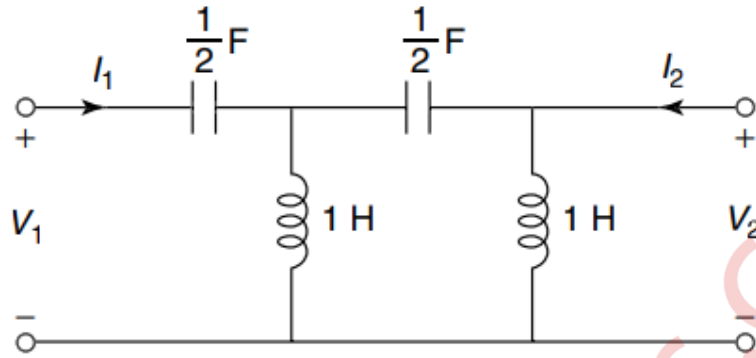
Q4 a Determine hybrid parameters of the given network. 10M



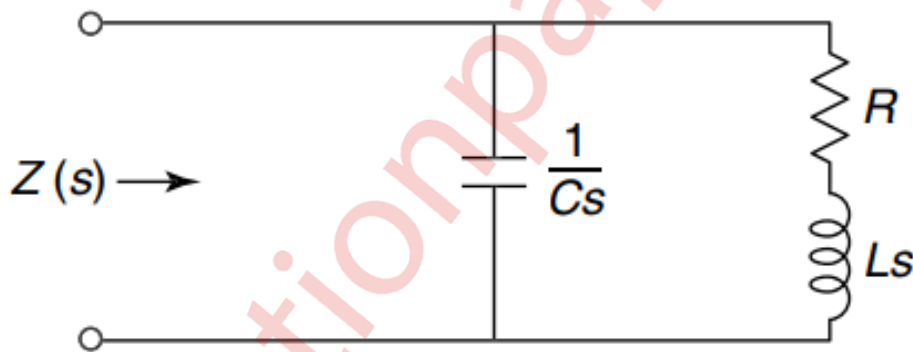
b The voltage $V(s)$ of a network is given by $V(s) = \frac{3s}{(s+6)(s^2+3s+3)}$. Plot its pole zero diagram and hence obtain $v(t)$. For the given network, poles and zeros of driving point function $Z(s)$ are, Poles: $(-1 \pm j4)$; zero: -2 . If $Z(j0) = 1$, determine the values of R , L and C . 10M



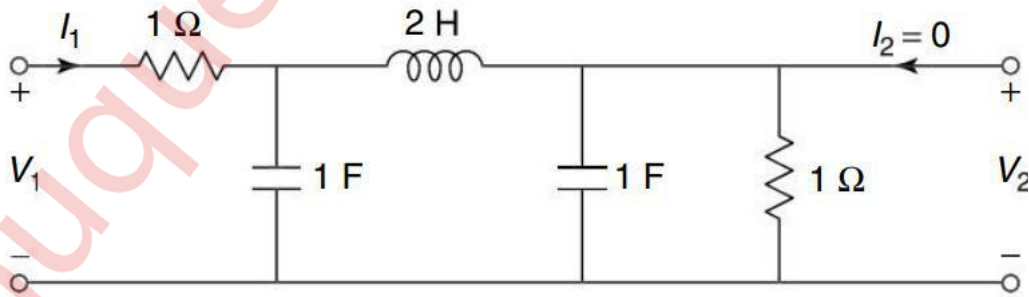
Q5 a For the given ladder network, determine the voltage transfer function V_2/V_1 10M



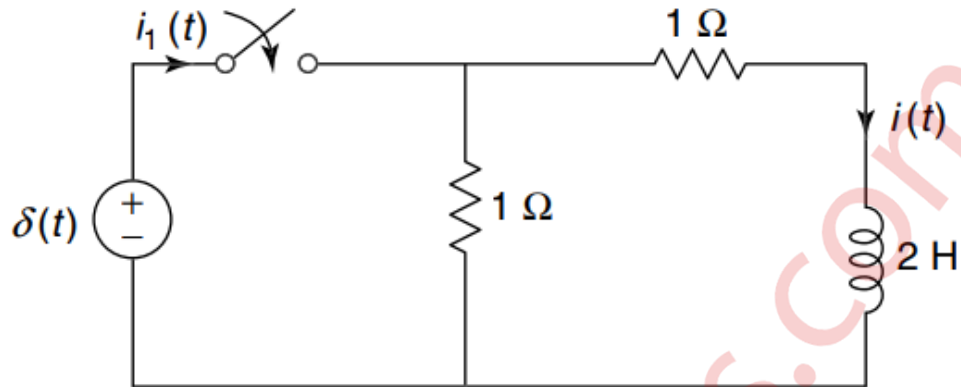b Determine the impulse response of the current $i(t)$ in the following network. **10M**



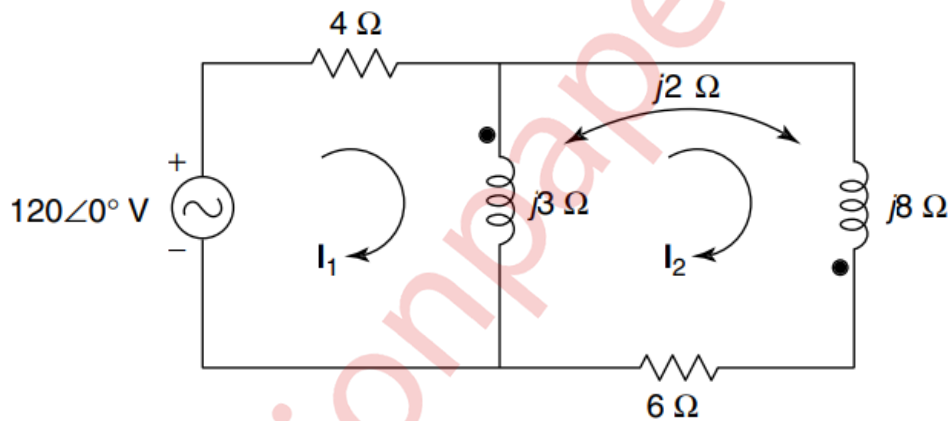Q6 a Find the current through the 6Ω resistor in the following circuit using mesh analysis. **10M**



b For the given network draw oriented graph and write the (i) reduced incidence matrix **10M**
 (ii) tieset matrix and (iii) fundamental cutset matrix.

