

Duration: 3hrs

Total Marks:80

- N.B.:** (1) Question No 1 is Compulsory.
(2) Attempt any three questions out of the remaining five.
(3) All questions carry equal marks.
(4) Assume suitable data, if required and state it clearly.

- 1 Attempt any FOUR [20]**
- a Convert $(1110010,1010)_2 = (?)_{16} (?)_8 (?)_{10} (?)_{\text{gray}} (?)_{\text{XS-3code}}$ [5]
 - b Implement 8:1 Mux with 4:1 Mux [5]
 - c What is latch? How a latch is different from flip flop? [5]
 - d Compare SRAM and DRAM [5]
 - e Compare PLA and PAL [5]
- 2 a** $F(p,q,r,s) = \sum m(0,2,5,6,8,9,11,13) + d(3,7,15)$ solve using K-map [10]
- b** Explain the sample and hold circuit. [10]
- 3 a** Explain the MasterSlave JK flipflop. [10]
- b** Explain the classification and characteristics of memory. [10]
- 4 a** Design the 4 bit Asynchronous counter. [10]
- b** Implement 3 bit binary to gray converter using NAND gate [10]
- 5 a** What is universal shift register ? Draw the circuit and explain its working. [10]
- b** Explain the 3 bit R-2R D/A converter [10]
- 6 a** Implement the T to D flip flop and JK to SR [10]
- b Short on any two: [10]**
- i) Dual slop A to D converter
 - ii) FPGA
 - iii) Shift Register
-