

(3 Hours)

[Total Marks: 80]

- N.B.: (1) Question No. 1 is **Compulsory**.  
 (2) Attempt any **three** questions out of the remaining **five**.  
 (3) Each question carries 20 marks and sub-question carry equal marks.  
 (4) Assume suitable data if required.

- Q1 Solve any four**
- (a) Perform the following operations by using 2's complement method, (5)  
 i) 46-23      ii) -46-25
- (b) Using two 74151s, design a 16 line multiplexer controlled by four data select control inputs. (5)
- (c) Describe the operation of 2 bit synchronous binary counter. (5)
- (d) Design divide by 4 counter using 7490. (5)
- (e) Write a code in VHDL to implement 2:1 MUX (5)
- Q2 (a) Simplify the following Boolean expressions** (10)  
 i)  $Y = \sum m(1,3,7,11,15) + d(0,2,5)$   
 ii)  $Y = \prod M(4,5,6,7,8,12).d(1,2,3,9,11,14)$   
 Minimize the following Boolean functions,  
 i)  $Y(A,B,C,D) = \sum m(1,3,5,8,9,11,15) + d(2,13)$   
 ii)  $Y(A,B,C,D) = \prod M(1,2,3,8,9,10,11,14).d(7,15)$
- (b) Discuss basic comparator operation. Draw the diagram and explain the working of a binary comparator for comparing two 4 bit binary strings. (10)
- Q3 (a) What is the difference between programmable logic array (PLA) and programmable array logic (PAL)? Explain PAL in details.** (10)
- (b) Describe a n bit binary ripple-carry adder showing typical carry propagation delays. (10)
- Q4 (a) Convert,** (10)  
 i) T flip flop into D flip flop  
 ii) D flip flop into J-K flip flop  
 iii) J-K flip flop into D flip flop  
 iv) J-K flip flop into T flip flop
- (b) Explain the working of CMOS NAND and NOR gates. Give its specifications. (10)
- Q5 (a) i) What is Hamming code? For the data bits 1011 construct even parity 7 bit Hamming code.** (10)  
 ii) If Hamming code received as 1111101. What is the corrected code? Assume even parity.
- (b) Explain Mealy and Moore Machines in details (10)
- Q6 Write short note on following,** (20)  
 i) Excess 3 Code  
 ii) De Morgan's Theorem  
 iii) Universal Shift Register  
 iv) CPLD and FPGA Architecture

\*\*\*\*\*