


Time: 3 hour

Max. Marks: 80

Q1 is compulsory.  
Attempt any three from Q2 to Q6.

- Q1 Solve any Five 4 Marks each**
- A Compare BJT and JFET.  
B Explain characteristics of Zener diode in Forward and Reverser bias. Comment on use of Zener diode as voltage regulator.  
C Differentiate between Small Signal amplifier and Large Signal amplifier.  
D Name the configurations of differential amplifiers. Draw any one. Also define parameters of differential amplifiers.  
E State and explain Millers Theorem.  
F What is thermal runaway? Comment on ideas to avoid it.  
G Explain construction and working of E-MOSFET. Also draw its drain and transfer characteristics.

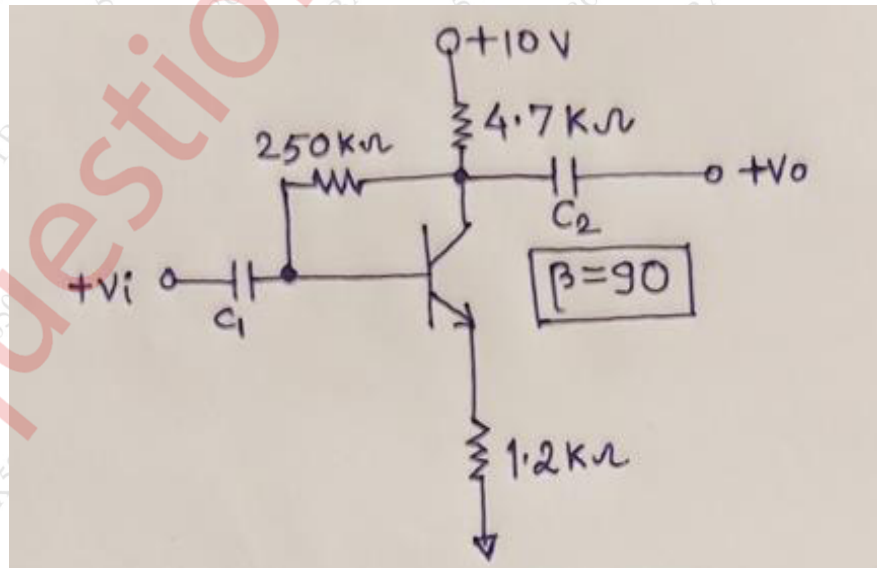- Q2 10 Marks each**
- A Draw a circuit diagram CE amplifier employing NPN transistor, RC coupling with emitter resistor completely bypassed, an appropriate load register  $R_L$ . Derive expression for its input impedance, output impedance, voltage gain and current gain.  
B Determine Quiescent magnitudes of  $I_c$  and  $V_{ce}$  for the given network.




**Q3**

**10 Marks each**

A


Determine the following for the network shown

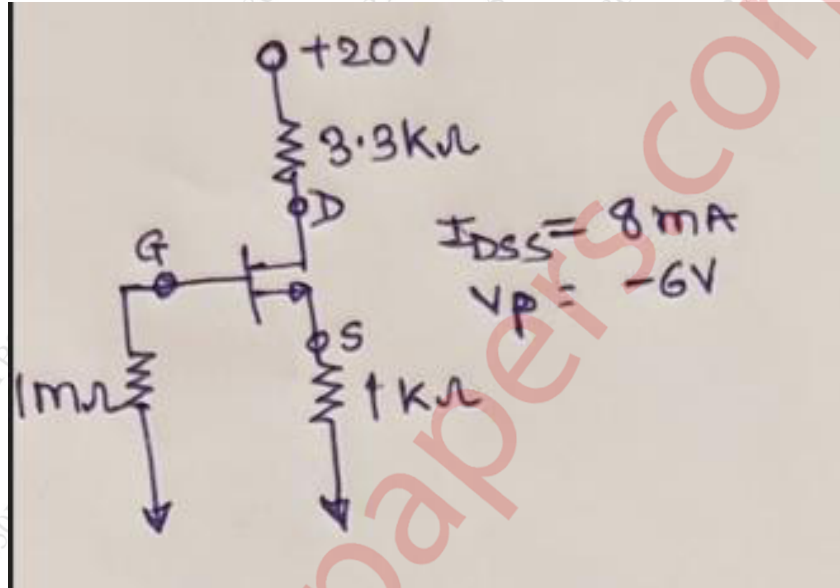i)  $V_{GSQ}$  ii)  $I_{DQ}$  iii)  $V_{DSQ}$  & iv)  $V_D$ .



B

Find  $|A_V|$ ,  $Z_i$  and  $Z_o$  For the given circuit.

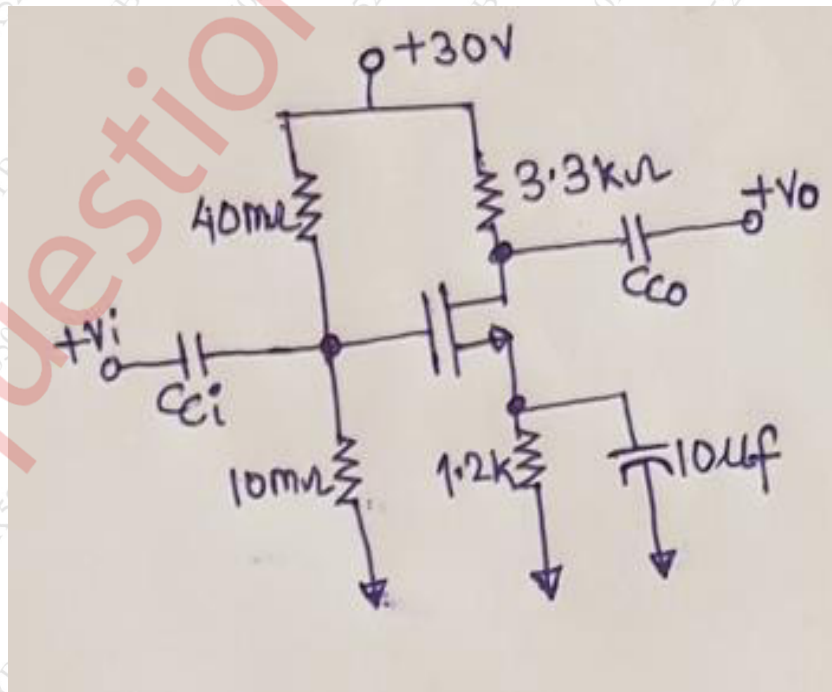

$V_{GS(Th)} = V_{TN} = 3V$ ,  $K = K_n = 0.4 \text{ mA/V}^2$  and  $r_o = r_d = 40 \text{ K}\Omega$

**Q4**


**10 Marks each**

- A Explain the concepts of heat sink in detail. Also mention equations for design considerations of heat sinks in power amplifiers.
- B State brief classification of power amplifiers. Derive equation for efficiency of a transformer coupled class- A power amplifier.

**Q5**

**10 Marks each**

- A Determine input impedance ( $Z_i$ ); output impedance ( $Z_o$ ); voltage gain ( $|A_v|$ ) and current gain ( $|A_{I1}|$ ) for network shown.

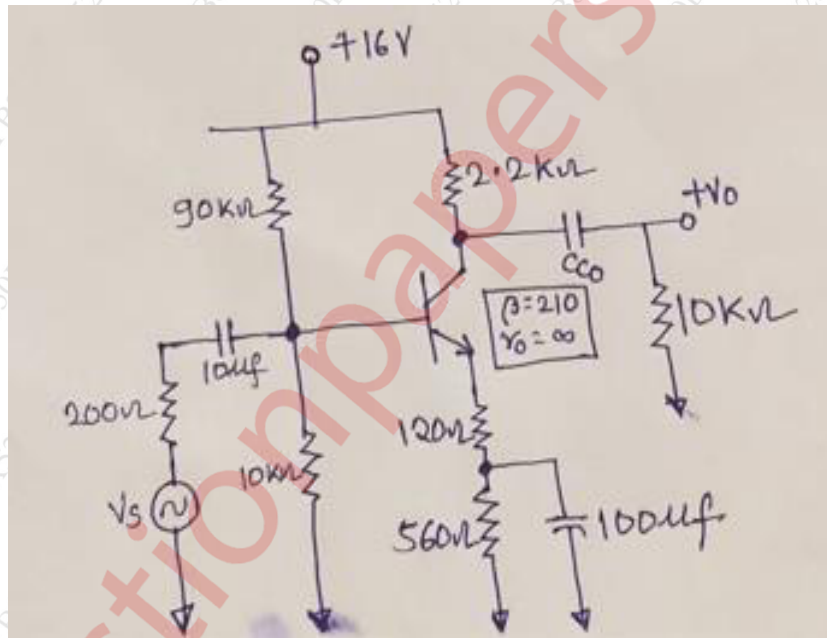

- B Draw a neat diagram of a MOS differential pair. Derive equation for CMRR for the same.

**Q6**

**Write short note on: [Any four]**

**5 marks each**

- A Compare in details DMOSFET and EMOSFET.
- B Explain concept of multistage amplifiers. State its advantages and disadvantages.
- C What do you understand by current mirror? Draw a two transistor (EMOSFET) current source and explain its operation.
- D What do you mean by crossover distortion in Class B power amplifiers? Can it be avoided? How?
- E Draw frequency response of Single Stage, RC coupled CS amplifier and comment on the effect of various external and internal capacitors.