


[Duration: 3 Hours]

[Max Marks: 80]

- N.B.:** (1) Question No 1 is Compulsory.
 (2) Attempt any three questions out of the remaining five.
 (3) All questions carry equal marks.
 (4) Assume suitable data, if required and state it clearly.

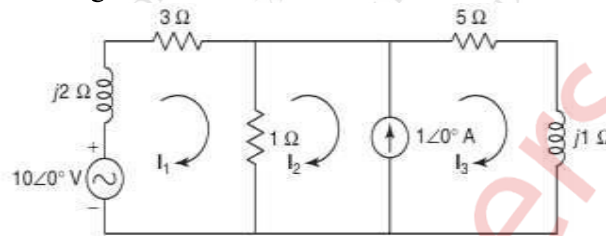
Q1 Solve any FOUR

- A** Find the current through $3\ \Omega$ resistor in the network. (05)




- B** The Z parameters of a two-port network are $Z_{11} = 20\ \Omega$, $Z_{22} = 30\ \Omega$, $Z_{12} = Z_{21} = 10\ \Omega$. Find Y and ABCD parameters. (05)

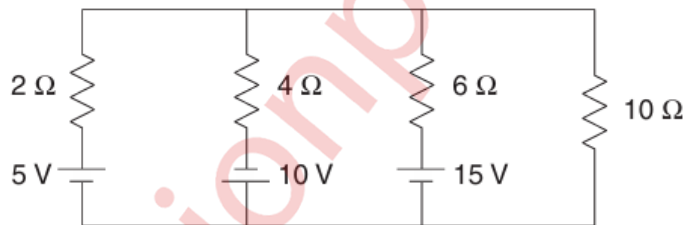- C** In the network shown, find the current through the $10\ \Omega$ resistor. (05)




- D** Test whether the polynomial. $P(S) = S^7 + 2S^6 + 2S^5 + S^4 + 4S^3 + 8S^2 + 8S + 4$ is Hurwitz (05)

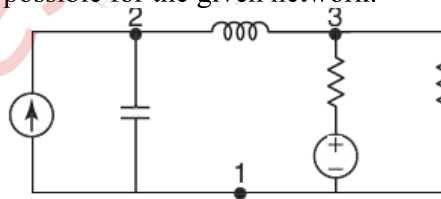- E** How many trees are possible for the given network. (05)




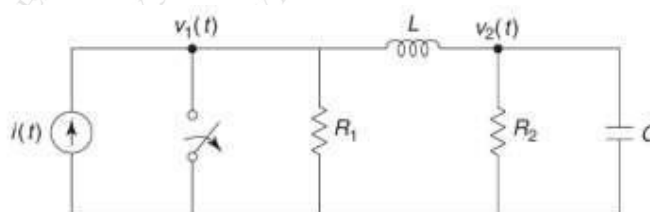Q2 Solve the following:

- A** The network shown in Figure has two independent node pairs. If the switch is opened at $t = 0$, Find $v_1, v_2, dv_1/dt$ and dv_2/dt at $t = 0^+$ (10)




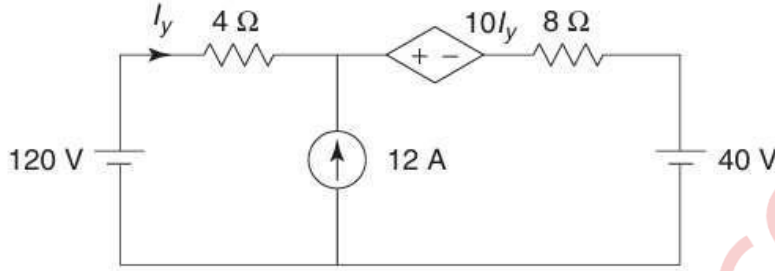B Find the current I_y using superposition theorem: (10)



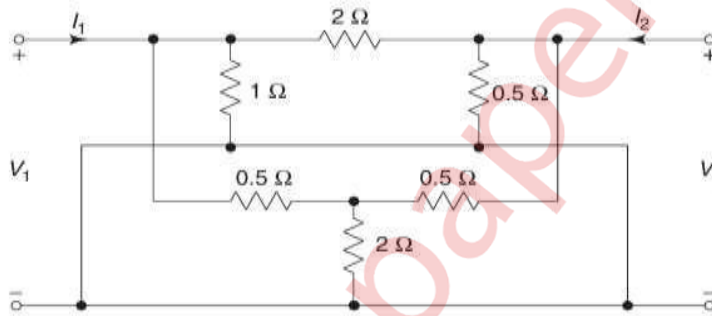Q3. Solve the following:

A Determine Y parameters for the network (10)




B Synthesize Foster – I and Foster – II forms of the LC impedance function (10)

$$Z(s) = \frac{(s^2 + 1)(s^2 + 3)}{s(s^2 + 2)}$$

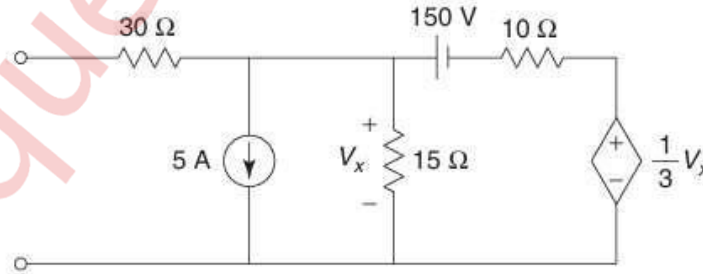Q4. Solve the following:

A Obtain the Thevenin's equivalent for the given network (10)



B Test whether $F(s) = \frac{2s^3 + 2s^2 + 3s + 2}{s^2 + 1}$ is positive real function. (10)


Q5. Solve the following:

A A network is shown in figure. The poles and zeros of the driving point function $Z(s)$ of this network are at the following places: **(10)**


Poles at $-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$

Zero at -1

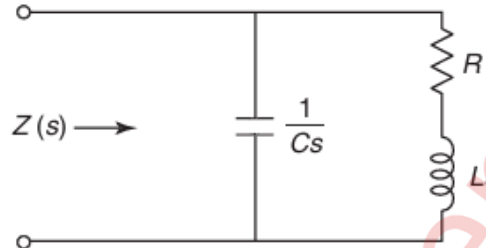If $Z(j0) = 1$, determine the values of R,L and C




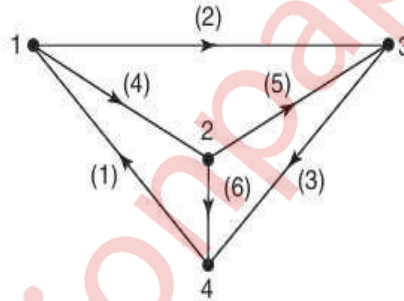B Find incidence matrix, tiset matrix and f-cutset matrix from given graph. **(10)**



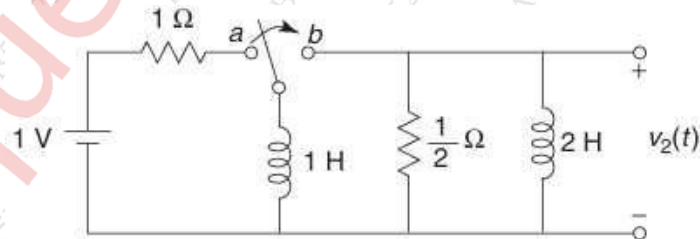Q6. Solve the following:

A In the network shown, switch is in position 'a' for long time. At $t = 0$, the switch is moved from a to b. Find $v_2(t)$. Assume that the initial current in 2H inductor is zero. **(10)**



B Find the condition of reciprocity and symmetry for ABCD parameters. **(10)**
