

06/06/2025 SE EXTC SEM-III C-SCHME DSD QP CODE: 10083098

(3 Hours)

Total Marks: 80

- N.B.**
1. Question No. 1 is **Compulsory**
 2. Out of remaining questions, attempt **any three**
 3. **Assume** suitable data if required
 4. Figures to the right indicate **full marks**

1. Attempt **any four**
 - (a) Perform subtraction using 2's complement method
i) $(68-24)_{10}$ ii) $(44-60)_{10}$ [5]
 - (b) State and prove De-Morgan's theorem [5]
 - (c) Convert the given Boolean expression to minterms $F(A,B,C,D) = Y = ABC + AC$ [5]
 - (d) Define and explain the following terms in case of logic families:
Figure of merit, Fan-in and Fan-Out, Current and Voltage parameters, Noise Margin [5]
 - (e) Write short notes on FPGA and CPLD [5]
2.
 - (a) Draw the block diagram of BCD adder using IC 7483 and show with example the addition of two BCD numbers [10]
 - (b) Develop a mod 6 Synchronous Counter using T F/Fs which counts in the sequence 0-1-2-3-4-5-0. Take care of lockout condition [10]
3.
 - (a) Minimize the following SOP using K-Map and implement using universal gates.
 $F = \sum m(0,2, 6,7,8,9, 10, 11, 12, 13) + d(14, 15)$ [10]
 - (b) Obtain the minimal expression using tabular method
 $F = \sum m(1,2, 3,5,6,7,8,9, 12, 13,15)$ [10]
4.
 - (a) What is shift register? Explain SISO type of shift register with an example [10]
 - (b) Implement a Full adder using PLA [10]
5.
 - (a) Draw and explain the working of a 4-bit Johnson counter with timing diagram [10]
 - (b) Sketch and explain the working of a 4-bit Asynchronous down counter using JK flip flop. Sketch each output with reference to clock [10]
6. Solve the following
 - (a) Give classification of semiconductor memories and explain DRAM in brief [5]
 - (b) Write VHDL code to build a 4:1 Multiplexer [5]
 - (c) Convert J-K-Flip Flop to T-Flip Flop [5]
 - (d) Convert J-K Flip-Flop to D-Flip-Flop [5]