04/06/2025 SE EXTC SEM-III C-SCHEME EDC QP CODE: 10087092

Duration: 3hours [Max Marks:80]

- N.B.: (1) Question No 1 is Compulsory.
 - (2) Attempt any three questions out of the remaining five.
 - (3) All questions carry equal marks.
 - (4) Assume suitable data, if required and state it clearly.
- 1 Attempt any FOUR

[20]

[5]


- a Calculate the reverse saturation current of a diode if the current at 0.2V forward bias is 0.1mA at a temperature of 25°C and the ideality factor is 1.5.
 - [5]

b Draw Drain and Transfer characteristics of E-MOSFET.

- [5]
- c What is Differential gain and Common mode gain related to differential amplifier And define CMRR.
- [5]


d Compare Small signal amplifiers and large signal amplifiers.

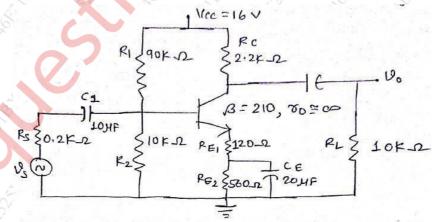- TX
- e Explain the concept of DC load line and AC load line w.r.t the CE amplifier output characteristics.
- 2 a Explain High frequency analysis of CS E- MOSFET amplifier with necessary equations and circuit diagrams. [10]
 - b Determine the input impedance, output impedance and voltage gain for the given circuit




3 a State different types of Coupling in multistage amplifiers with suitable [10] diagrams and explain any one coupling method with its advantages and disadvantages.

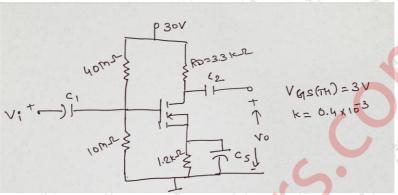b Determine output voltage of below given network if input voltage vi = 0.8mv and rd=40 Kohm



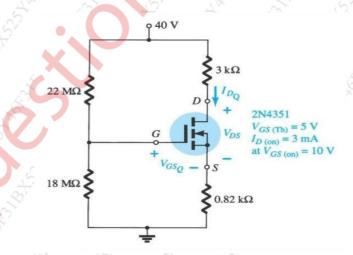- 4 a State and explain Miller effect. Derive Miller input impedance and Miller output impedance in case of capacitive reactance. [10]
 - b What is cross over distortion in class B Power amplifier and how it is overcome by diode biasing of class AB Power amplifier.
- 5 a Find the value of I_{DQ} , V_{GSQ} and V_{DSQ} for given circuit. [10]



- b Draw and explain high frequency model for BJT in CE configuration. [10]
- 6 a The cascading of amplifiers increases the gain but it reduces bandwidth. [10]
 Justify with suitable equations and diagram/Plot.
 - b Draw and explain DC transfer characteristics of MOSFET differential amplifier. Derive expression describing DC transfer characteristics of MOSFET differential amplifier.

87092