

10/06/2025 SE EXTC SEM-III C-SCHEME NT QP CODE: 10083018

Time: 3 Hours

Max. Marks: 80

Question No. 1 Compulsory


Question No. 2 to Question No. 6 Solve any Three

Q1 Solve any Four out of Five

5 marks each

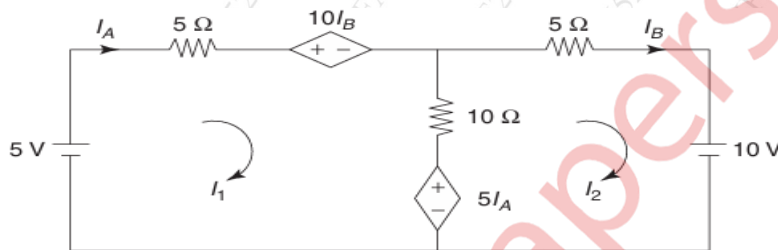(20)

A Determine the branch currents in the network shown



B Derive condition of symmetry and reciprocity for h parameters

C Obtain the pole zero plot of the following function

$$\frac{(S+1)^2(S+5)}{(S+2)(S+3+j2)(S+3-j2)}$$


D Test whether the polynomial $P(s) = S^4 + S^3 + 3S^2 + 2S + 12$ is Hurwitz.

E The reduced incidence matrix of an oriented graph is given below. Draw the oriented graph and write fundamental tiset matrix and cutset matrix.


$$A = \begin{bmatrix} 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & -1 & -1 & -1 \\ -1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

Q2

10 marks each

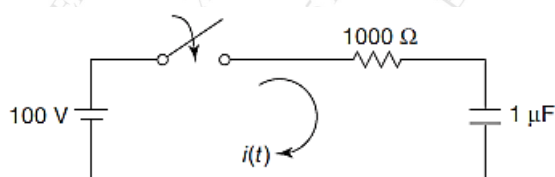A In the network, the switch is closed at $t = 0$. With the capacitor uncharged, find value for i , di/dt , d^2i/dt^2 at $t = 0^+$ 

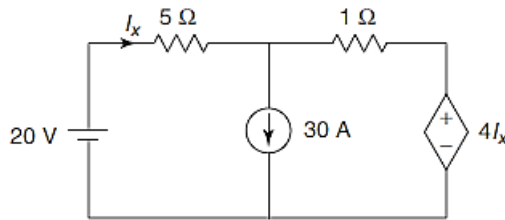
B Find the current I_x using superposition theorem:



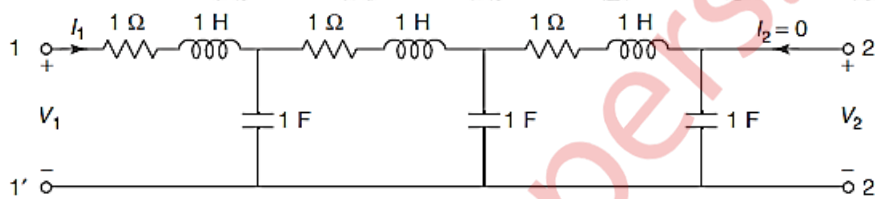Q3.

10 marks each

A For the ladder network of Fig, find the driving point-impedance at the 1 – 1' terminal with 2 – 2' open.



B Synthesize in Cauer – I and Cauer – II form

$$Z(s) = \frac{(s+2)(s+6)}{2(s+1)(s+3)}$$

Q4.

10 marks each

A Test if $F(s) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$ is a positive real function.

B Currents I_1 and I_2 entering at Port 1 and Port 2 respectively of a two-port network are given by the following equations:

$$I_1 = 0.5V_1 - 0.2V_2$$



$$I_2 = -0.2V_1 + V_2$$

Find Y, Z and ABCD parameters for the network.

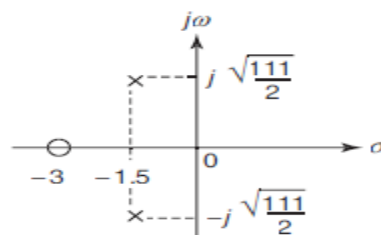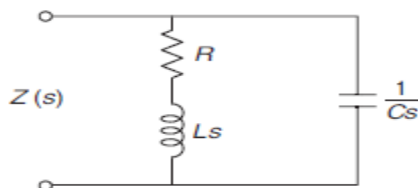
Q5.

10 marks each

A A network and its pole- zero configurations are shown. Determine the values of R, L and C if $Z(j0) = 1$



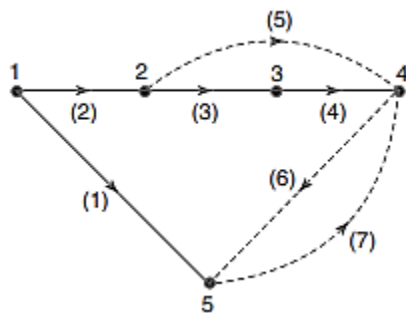- B Find reduced incidence matrix, Tie set matrix and Cutset matrix of given graph-



Q6.

10 marks each

- A For the network shown switch is closed at $t = 0$. Determine the current $i(t)$ assuming zero initial conditions.



- B Find the value of resistance R_L in network for maximum power transfer and calculate the maximum power.

