

9/12/2024 EXTC SEM-IV C SCHEME LIC QP CODE: 10064354

Time: 3 Hours

Total Marks: 80

N.B.:

- 1) Question No.1 is compulsory
- 2) Solve any three from the remaining five.
- 3) Figures to the right indicate full marks.

Q. 1 Attempt any four questions.

- A) Compare Active filters and Passive filters. [5]
- B) List the specifications of a power supply and explain the following:
Load Regulation, Line Regulation and Ripple Rejection. [5]
- C) Explain inverting type ZCD with input-output waveforms. [5]
- D) Write note on Pulse Width Modulator. [5]
- E) Explain the block diagram of Op-Amp IC 741. [5]

- Q. 2** A) Design a practical differentiator to differentiate the input sine wave signal.
Assume $f_a = 1$ kHz, $C_1 = 0.1 \mu\text{F}$ and $R_1 = 82$ Ohms. [10]
- B) Design Second order Butterworth High Pass filter with Cut off frequency 10 kHz.
Draw the designed circuit and frequency response. [10]

- Q. 3** A) Design square wave generator using Op-Amp to generate a perfect square of 50% duty cycle with output frequency of 1 kHz. Assume the feedback factor to be 0.1. Also draw the output waveform and waveform across the capacitor. [10]
- B) Draw and explain working of RC-phase shift Oscillator and derive the expression for output frequency. [10]

- Q. 4** A) Explain the Astable Multi-vibrator using IC 555. Derive the expression for T_c and T_d and duty cycle. Draw the corresponding waveforms. [10]
- B) Design a voltage regulator using IC 723 to give output voltage $V_o = 5$ V and output current of 2 A. [10]

- Q. 5** A) What is an Instrumentation Amplifier? Draw a neat diagram of three-op-amp I A. Derive its output voltage equation. [10]
- B) With the help of a neat diagram, input-output waveforms and voltage transfer characteristics explain the working of an Inverting Schmitt Trigger. Derive the expression for the Upper and Lower threshold levels. Explain how to vary these levels. [10]

Q. 6 Write short notes on: (Attempt any four)

- A) The Voltage follower (Buffer). [5]
- B) Wein-Bridge Oscillator using op-amp [5]
- C) Three Terminal IC Voltage Regulators [5]
- D) Phase Locked Loop (PLL) with one application [5]
- E) Window detector [5]