

(3 Hours)

[Total Marks: 80]

- N.B.: (1) Question No. 1 is **Compulsory**.  
(2) Attempt any **three** questions out of the remaining **five**.  
(3) Each question carries 20 marks and sub-question carry equal marks.  
(4) Assume suitable data if required.

QP-10066428

1. (a) Evaluate the Following Operation in BCD (5)  
a)  $(56)_{10} + (23)_{10}$   
b)  $(48)_{10} + (26)_{10}$   
(b) Define A) Noise Margin (5)  
B) Fan Out  
(c) Compare Moore and Mealy Circuits (5)  
(d) Explain core features of Verilog language. (5)
2. (a) Design and Implement Full subtractor circuit using IC74151(Multiplexer) (10)  
(b) Design and Implement sequence detector circuit for 1011 (non overlapping sequence) using JK flip-flop. (10)
3. (a) Design Mod-100 counter using IC7490 (10)  
(b) Write Verilog code for Full adder. (10)
4. (a) Design Mod 10 Asynchronous counter using T Flip-Flop. (10)  
(b) Design Mod-10 counter using IC 74163 (10)
5. (a) Explain the interfacing of a TTL gate driving CMOS gates and vice versa (10)  
(b) Draw a neat circuit diagram of four bit Twisted Ring Counter with initial state 0000 and relevant output waveforms. (10)
6. (a) Convert the following (10)  
a) Convert D Flip-Flop into T Flip-Flop b) JK flip-flop to D flip-flop  
(b) Explain XC 9500 CPLD architecture with neat clean diagram. (10)

\*\*\*\*\*