


[Time : 3 Hours]

[Total Marks:80]


- N.B.:** (1) Question No 1 is Compulsory.
 (2) Attempt any three questions out of the remaining five.
 (3) All questions carry equal marks.
 (4) Assume suitable data, if required and state it clearly.

QP-10066757

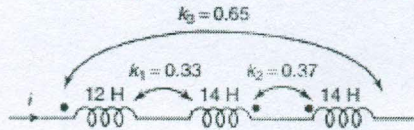
- 1 Attempt Any Four. [20]
 a Explain various types of filters. [05]
 b Write the properties of a Hurwitz Polynomial [05]
 c List the type of damping in a series R-L-C Circuit and mention the condition for each damping. [05]
 d Prove the condition of Reciprocity of H parameters [05]
 e Find the Equivalent Inductance of the network shown in figure [05]



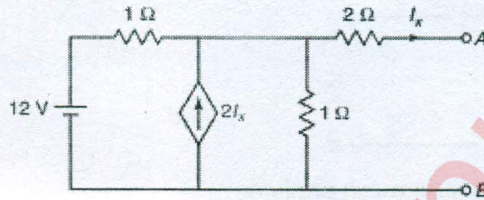
- 2 a Find V_{th} and R_{th} between terminals A and B [10]



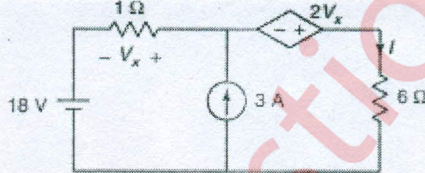
- b Find the current in 6 Ω resistor by superposition theorem [10]



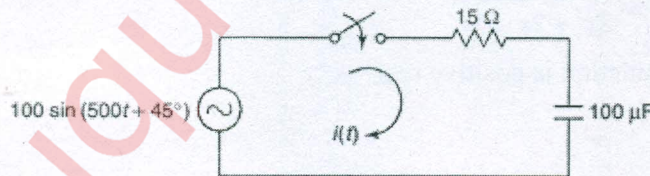
- 3 a In the network shown in figure a sinusoidal voltage $v = 100 \sin(500t + \theta)$ volts is applied to the circuit at a time corresponding to $\theta = 45^\circ$, obtain the expression of $i(t)$ [10]



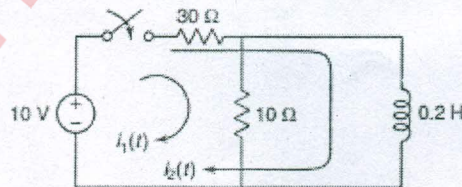
- b The switch in the network is closed at $t = 0$, find $V_2(t)$ for all $t > 0$. Assume zero initial current in the inductor [10]



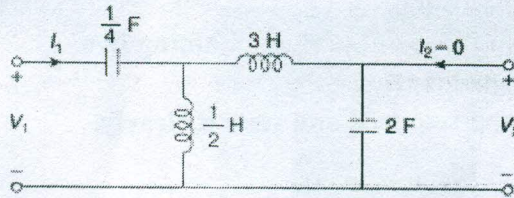
- 4 a For the network shown in figure Find V_1/I_1 , V_2/V_1 and V_2/I_1 [10]



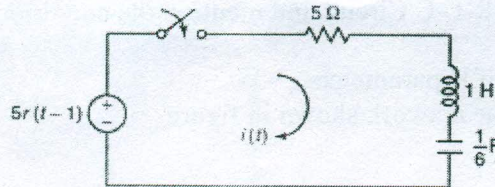
- b Determine the current $i(t)$ for the network shown in figure when the switch is closed at $t = 0$ [10]



- 5 a [10]

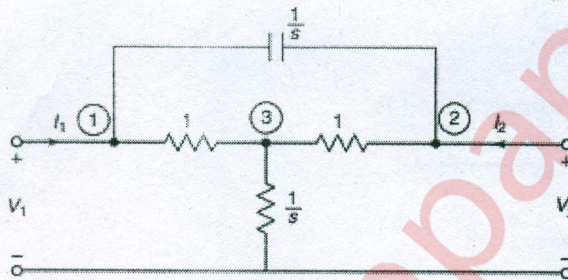

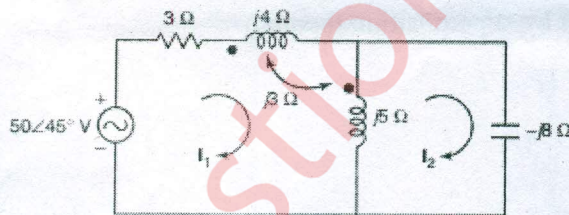- b Find the current through the capacitor using mesh analysis [10]



- 6 a Realise Cauer forms of the following LC impedance function: [10]

$$Z(s) = \frac{10s^4 + 12s^2 + 1}{2s^3 + 2s}$$

- b Test whether the given function is positive real [10]

$$F(S) = \frac{s^3 + 6s^2 + 7s + 3}{s^2 + 2s + 1}$$
