


Duration: 3 Hours

[Max Marks: 80]


- N.B. : (1) Question No 1 is Compulsory.
 (2) Attempt any three questions out of the remaining five.
 (3) All questions carry equal marks.
 (4) Assume suitable data, if required and state it clearly.

QP-10065597

- 1 Attempt any FOUR [20]
 a Draw energy band diagram of pn junction diode under forward bias and reverse bias. [5]
 b Explain positive clamper circuit with proper waveforms. [5]
 c Draw output characteristics of transistor in CB and CE mode [5]
 d In dc analysis circuit capacitors acts as open circuit. - Justify [5]
 e Which biasing method can not be used for DMOSFET and why? [5]
- 2 a Determine Q-point, VB, VC and VE for following circuit diagram and draw dc load line. [10]

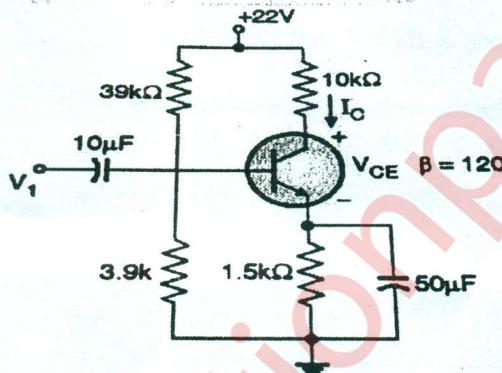


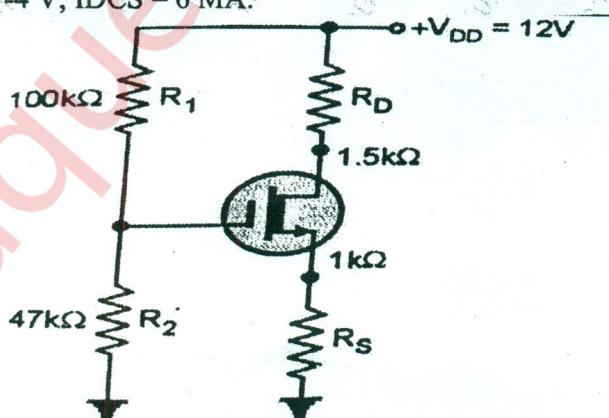- b Explain construction, operation and V/I characteristics of EMOSFET. [10]
- 3 a Determine VGSQ, IDQ & VDSQ for following circuit In Fig. [10]
 $V_P = -4 \text{ V}$, $ID_{CS} = 6 \text{ mA}$.



- b Explain operation of Bridge rectifier & draw the o/p waveform for dc o/p voltage and current [10]

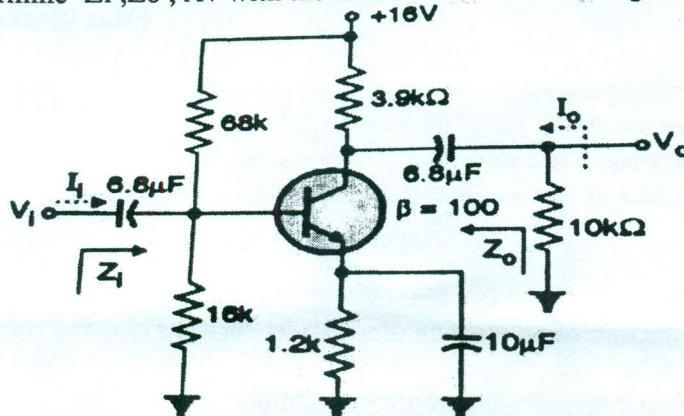- 4 a Determine Z_i , Z_o , A_v with the load & A_v with load for given circuit diagram [10]



- b Draw CS amplifier circuit and derive the equation for voltage gain. [10]
- 5 a Write short notes (any two) [10]
- i. Zener Diode as a Voltage Regulator
 - ii. L Filter
 - iii. Early effect in BJT
- b Explain working of PN junction diode & its V-I characteristics. [10]
- 6 a Design Single stage CE amplifier for the following specifications [15]
- $A_v \geq 100$, $V_o = 2.5$ v, $F_L = 20$ Hz, $S = 10$. use BC147A transistor.
- b Compare CB , CC , & CE amplifier. [05]