

SE(ELEX.) / Sem-III / R-20 / C Scheme / DLC

(3 Hours)

[Total Marks: 80]

Note: (1) Question No. 1 is **Compulsory**.(2) Attempt any **three** questions out of the remaining **five**.


(3) Each question carries 20 marks and sub-question carry equal marks.

(4) Assume suitable data if required.

- Q.1: (a) Convert T flip flop to D flip flop. (5)
 (b) Design a circuit using 2:1 MUX to implement 2-input NAND Gate. (5)
 (c) Generate 7-bit even parity Hamming code for data 1101. (5)
 (d) Write a Verilog code for Half Subtractor using Gate-level modelling (5)
- Q.2 (a) Draw and explain 5-bit Comparator using IC 7485. (10)
 (b) Design MOD-8 Synchronous Counter using JK-FF. (10)
- Q.3 (a) Construct 2 input CMOS NAND logic gate and explain. (10)
 (b) Design 1- digit BCD Adder using IC 7483. (10)
- Q.4 (a) Using K-map reduce given logical function and implement using NAND gates only: (10)

$$F(A,B,C,D) = \sum m(1,2,3,6,8,9,11,14) + d(0,7,10,15)$$

  (b) Analyze the given FSM and obtain the state diagram for the same (10)



- Q.5 (a) Implement function $F1 = \sum(4,5,7)$ and $F2 = \sum(3,5,7)$ using PLA (10)
 (b) Draw a circuit diagram of 4-bit SISO shift register and also give its output waveforms. (10)
- Q.6 (a) Design Mealy overlapping sequence detector using D-FF to detect 1011. (10)
 (b) Write a Verilog code for Full Adder using behavioral modelling style (10)

ap code 85294

 prog. code :
 IT01133