


Time Duration: 3 Hours

Maximum Marks: 80 Marks



- N.B. : (1) Question No 1 is compulsory.  
 (2) Attempt any three questions out of the remaining five.  
 (3) All questions carry equal marks.  
 (4) Assume suitable data, if required and state it clearly.

- 1 Attempt any FOUR [20]
  - a Explain the transfer characteristics of N-channel JFET with a neat sketch & define the term 'transconductance'.
  - b Compare full-wave bridge type rectifiers & full-wave center-tapped rectifiers.
  - c With neat sketch describes the operation of the inductor (L) filter with appropriate waveforms.
  - d Explain the concept of DC load line & Q - Point in bipolar junction transistor (BJT).
  - e Describe any two types of clamper circuits with a neat diagram along with input & output waveforms.
- 2 a Describe the working or operation of a center-tapped type full wave rectifier with a neat sketch. Draw the output voltage waveforms & mention the expression for DC or average output voltage. [10]
- b Identify the electronic circuit as for which the following diode can be used as shown below. Describe its operation for both, varying load resistance with a constant DC supply voltage & a varying DC supply voltage with a constant load resistance. [10]

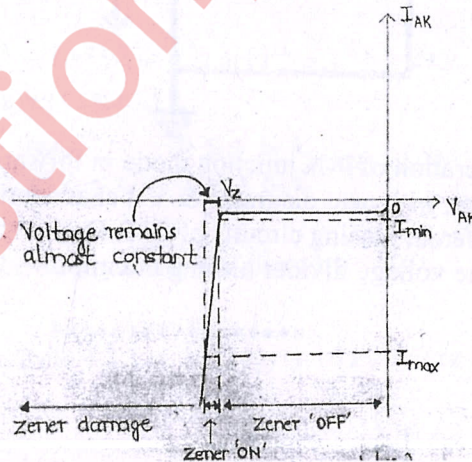

- 3 a Explain how a PN junction is formed with a neat diagram. [10]
- b Explain with the help of neat diagram construction, working & V-I characteristics of N - channel enhancement MOSFET. [10]
- 4 a Draw a circuit diagram of common source (CS) E-MOSFET amplifier, derive equation of voltage gain ( $A_v$ ), input resistance ( $R_i$ ) & output resistance ( $R_o$ ). [10]
- b For small signal amplifier in common emitter (CE) BJT configuration using voltage divider biasing perform small signal (AC) analysis using the hybrid -  $\pi$  model. [10]


Qp code:

82771

Page 1 of 2

Prog. code: 1T01133

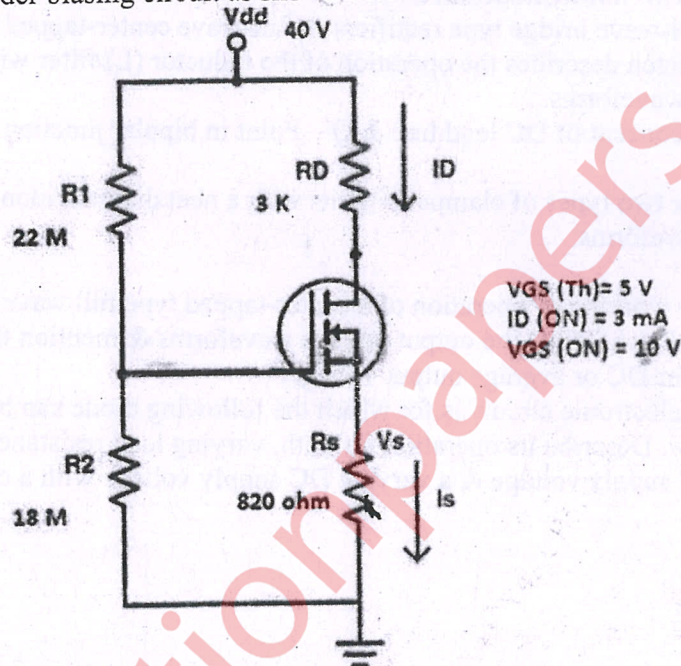- 5 a With a neat sketch, write a short note on a solar cell describing its structure or construction, working & V-I characteristics. Mention few real-life applications of solar cells [10]
- b Calculate the operating point (Q – Point) of the following E-MOSFET using the voltage divider biasing circuit as shown below. [10]



- 6 a Describe the operation of P-N junction diode in forward bias & reverse bias mode of operation with neat diagrams & V-I characteristics. [10]
- b Draw all the different biasing circuits of BJT. Derive the expression of stability factor (SI) for the voltage divider biasing circuit. [10]

\*\*\*\*\*