

S.E. / ELX / Sem-IV / CBCGS / R-U / 'c' scheme / Sub:- EDG-II

S.H. 2024

[Time : 3 Hours]


[Total Marks:80]

Date: 04/12/2024

CP. Code: 10066737


- N.B.:** (1) Question No 1 is Compulsory.
 (2) Attempt any three questions out of the remaining five.
 (3) All questions carry equal marks.
 (4) Assume suitable data, if required and state it clearly.

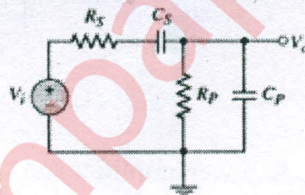1. Attempt any FOUR [20]
- Draw block diagram of negative feedback amplifier and derive equation for gain.
 - Compare RC phase shift oscillator and Wien bridge oscillator.
 - Draw and explain different types of differential amplifier configurations.
 - Explain how power amplifier is different from voltage amplifier
 - What are the different types of power amplifiers along with their power efficiency.
2. a Determine the corner frequencies and bandwidth of a passive circuit containing two capacitors. Consider the circuit shown in Figure 7.10 with parameters $R_S = 1k\Omega$, $R_P = 10k\Omega$, $C_S = 1\mu F$, and $C_P = 3pF$ [10]



- b Write a short note on FET Cascode amplifier (CS-CG). [10]
3. a Explain voltage series negative feedback amplifier with help of block diagram and derive expression for R_{if} , R_{of} and A_f . [10]
- b Write a short note on Crystal oscillator. Describe its advantages, disadvantages and applications. [10]
4. a What are the different methods to improve CMRR. Explain any one. [10]
- b Draw and explain transformer coupled Class-A Power amplifier and derive the maximum power conversion efficiency for the same. [10]
5. a Explain Miller's theorem with respect to capacitance. Derive the necessary expressions. [10]
- b Explain what is a multistage amplifier? Explain the different types of coupling methods. [10]
6. a Consider a MOSFET differential amp with the configuration as shown in the figure. Assume $K_{n1} = 1 \text{ mA/V}^2$, $I_Q = 0.587 \text{ mA}$ and $\lambda = 0.01 \text{ V}^{-1}$ for M_4 . [10]

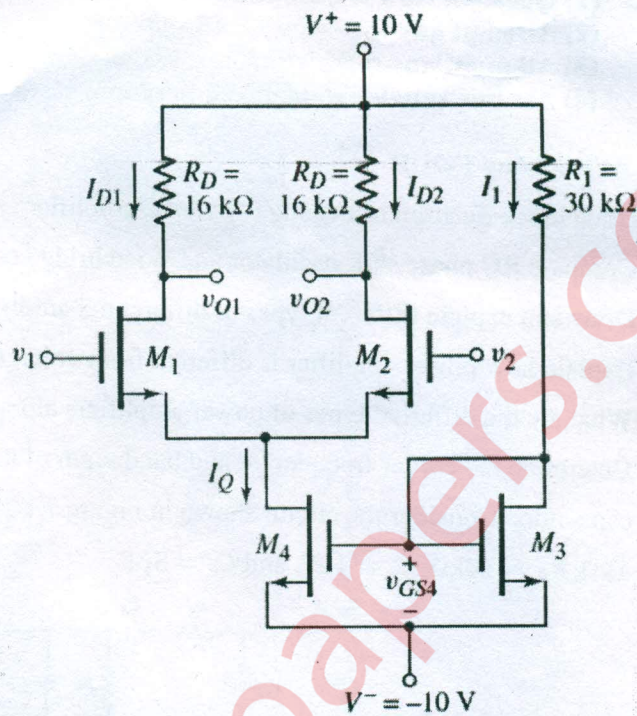Determine the output resistance of current source, differential-mode voltage gain, common-mode voltage gain and CMRR for the differential amplifier.



- b Explain Class-B power amplifier and crossover distortion. Drive expression for its efficiency. [10]
