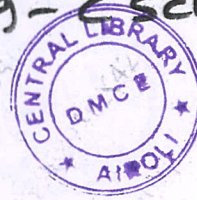


E(ELX.) / SEM-V / LIC / R-19 - e scheme / 09/06/25.



Time: 3 Hours

Max. Marks: 80

- NB:** 1. Question No. 1 is compulsory and solve any **THREE** questions from the remaining questions  
 2. Assume suitable data if necessary  
 3. Draw clean and neat diagrams

**Q.1** Attempt the following questions. (20)

- Draw block diagram of OPAMP and explain function of each block. 5
- Draw circuit diagram and frequency response characteristics of first order Low pass filter and explain its operation? 5
- Explain why OPAMP is called linear IC? 5
- Compare ideal and practical Differentiator circuit? 5

**Q.2.a.** Design a 2nd order KRC high Pass Filter with a cut-off frequency of 4 kHz and a Quality Factor (Q) of 3. 10

b. Draw and explain the working of a RC PHASE SHIFT Oscillator using an Op-Amp. State formula for frequency of oscillation. 10

**Q.3.a.** Explain with necessary diagrams and waveforms the principle of operation of a Astable Multivibrator using IC 555. 10

b. Design an IC 555 Astable Multivibrator for an output frequency of 1.2 kHz with a duty cycle of 60%. 10

**Q.4.a.** Explain with a circuit diagram the principle of operation of a any one method of ADC. 10

b. With a neat circuit, explain the working of the Weighted resistor type Digital to Analog Converter (DAC). 10

**Q.5.a.** Draw the circuit diagram and explain the operation of a Triangular Wave Generator using Op-Amp. Also, describe the modifications required to obtain a Sawtooth Wave Output. 10

b. Explain internal diagram of power amplifier LM 380. 10

**Q.6** Write notes on following 20

- Peak detector
- Voltage to current converter.

**Q. P. Code :-**  
86940

**Program Code:-**

1TD1135.