

B.E. / BLX / Sem-VIII / CBCRS / R-19 / 'C' Scheme / Subj: APE / S.H. 2024

Date: - 04/12/2024

Q.P. Code: - 10065460

Time: 3 hours

Max. Marks: 80

N.B. (1) Question no.1 is compulsory.

(2) Attempt any three questions from the remaining five questions.

(3) Assume suitable additional data if required.

(4) All questions carry equal marks.

- 1 Answer any four of the following.
- | | | |
|---|--|----|
| a | Outline the goal of the EMC test. State the EMC issues and state how those issues are resolved. | 5 |
| b | Compare 120 degree and 180 degree conduction modes in bridge inverters. | 5 |
| c | What are the advantages of SVM over the conventional sine wave PWM? Explain. | 5 |
| d | Describe the methods for PI control for AC-DC converters. | 5 |
| e | Differentiate between microgrid and smart grid. | 5 |
| 2 | a Explain the working of 3 phase full wave-controlled rectifiers with R load for angle of 60 degree. | 10 |
| | b Draw and explain speed torque curves for an AC motor and derive the equation for torque. | 10 |
| 3 | a Explain 180-degree conduction mode in three phase VSI. | 10 |
| | b Explain SVM inverter with waveforms. | 10 |
| 4 | a Derive the state space averaged model for a DC-DC buck converter and hence obtain the steady state transfer function, V_o/V_{in} | 10 |
| | b Explain anti saturation protection circuit for IGBT. | 10 |
| 5 | a Derive the FOH and SOH model for AC-AC converter. | 10 |
| | b Explain Slip power recovery schemes. | 10 |
| 6 | Write short note on (Any two): | |
| | a Applications of Induction heating in power electronics | 10 |
| | b Inverter interfacing control strategies for transferring solar energy to grid. | 10 |
| | c Distributed energy sources | |
| | d Electric braking of DC motors | |
