

Time: 2 Hours


Max Marks: 60

N.B.:

- (1) Question No.1 is compulsory.
- (2) Attempt any THREE questions from remaining FIVE questions.
- (3) Assume suitable data if necessary and mention the same clearly.
- (4) Figures on the right indicate the marks.

- | | | Marks |
|-----|---|-------|
| Q.1 | a. Write formulas for Delta to Star and Star to Delta transformation. | 3 |
| | b. An alternating current of frequency 50 Hz has a maximum value of 12 A. Find (i) Equation for instantaneous value of current and (ii) Time taken to reach 9.6 A for the first time. | 3 |
| | c. What is the efficiency of transformer? | 3 |
| | d. State the function of each constructional part of a DC motor. | 3 |
| | e. Write applications of LED. | 3 |
| Q.2 | a. Using Superposition theorem, find voltage across 4 Ω resistor. | 10 |
-
- | | | |
|-----|--|----|
| | b. Explain the working principle of three phase induction motor. | 5 |
| Q.3 | a. A coil consumes 1 KW power from 50 Hz single phase ac supply and volt-ampere input is 2 KVA. If value of resistance of coil is 10 Ω then find the following parameters with respect to a coil.
(i) Value of inductance, (ii) Phase angle, (iii) Power factor, (iv) Impedance, (v) Voltage and Current equations, (vi) KVAR | 10 |
| | b. Draw and explain the V-I characteristics of a Zener diode | 5 |
| Q.4 | a. State and prove the Maximum power transfer theorem. Derive the formula of Maximum power delivered. | 5 |
| | b. Explain the application of BJT as an amplifier. | 5 |
| | c. Three similar coils each having a resistance of 5 Ω and an inductance of 0.02 H are connected in star to a 440 V, 50 Hz, 3-phase supply. Calculate (i) line current and (ii) active and reactive power | 5 |

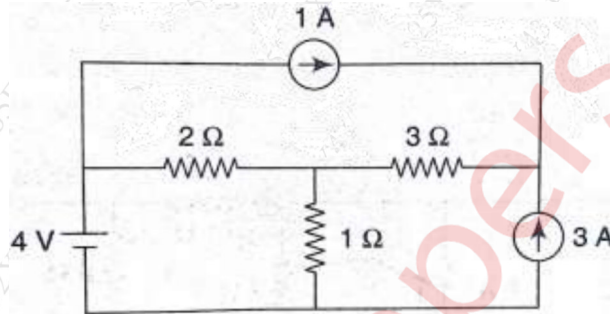- Q.5 a. Explain the working principle and transformation ratio of a single-phase transformer. 6
- b. Write short note on any one: 4
- (i) Single phase induction motor
- (ii) BLDC motor.
- c. Two impedances of $12 + j16 \Omega$ and $10 - j20 \Omega$ are connected in parallel across 230 V, 50 Hz, single phase ac supply. Find admittance, current and power factor of each branch. 5
- Q.6 a. Find current flowing through 1Ω resistance by Node analysis. 6



- b. State the necessary condition for resonance in a series circuit. Compare series and parallel resonance. 5
- c. Write a short note on FET. 4